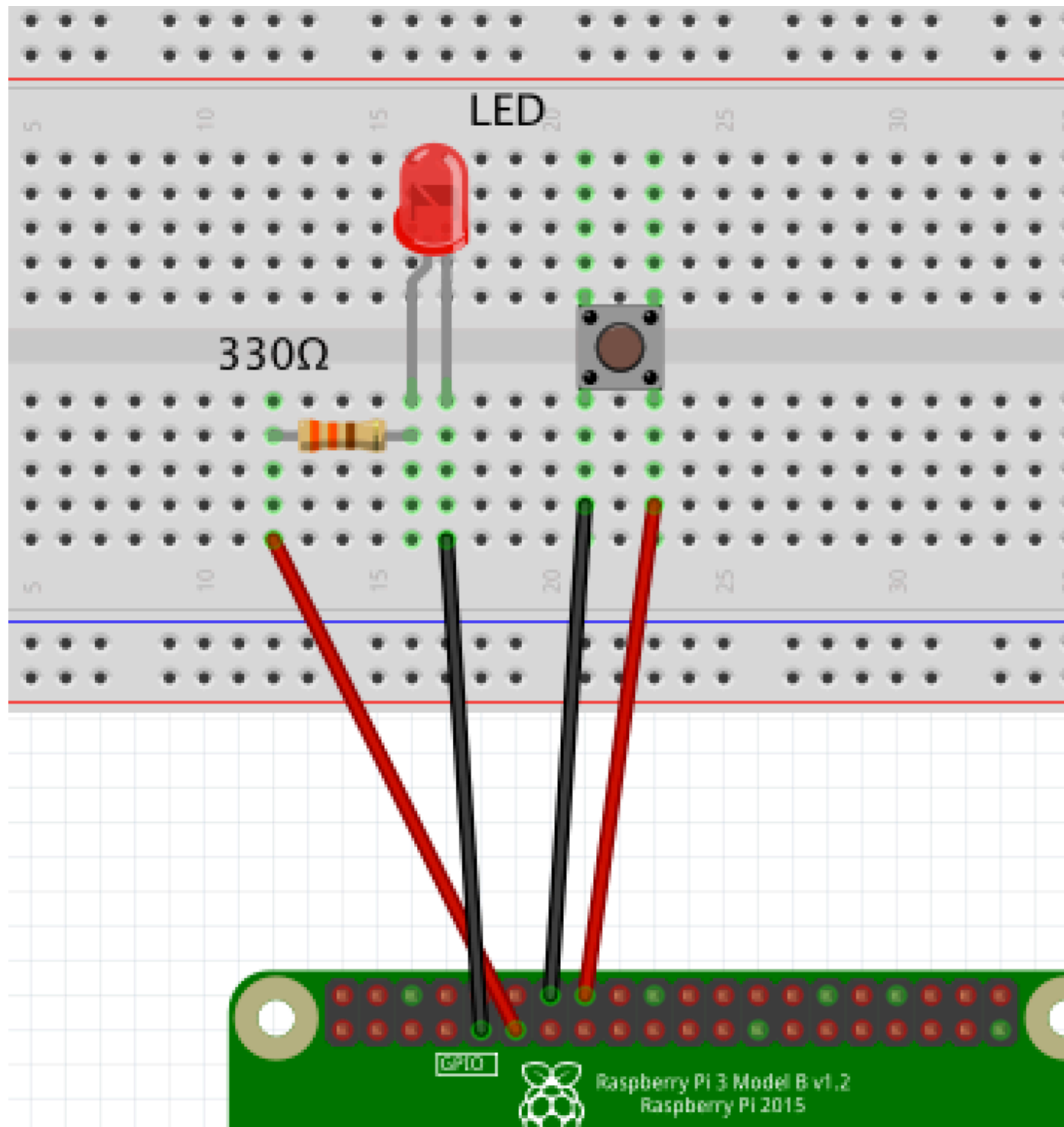


# Using a button to control an LED

## **Additional parts needed**

- LED
- 330  $\Omega$  resistor
- Push button switch
- Connecting wires
  - 4 Male-Female wires

# Using a button to control an LED



Pin#	GPIO#	Connection
14	GND	Button pin
16	GPIO23	Button pin
11	GPIO17	Resistor to LED Anode
9	GND	LED Cathode